

INTRODUCTION

This is the first lab not based on the book *Getting Started with MicroPython*. In this lab you are going to explore some of the common usages of capacitors in circuits. One use is to use an RC circuit to time events or set the oscillation time of a circuit. A second usage is to filter signals in frequency, and a third usage is to *decouple* DC, AC, and noise signals from each other. This covers a lot of territory, so let's get started!

CAPACITORS FOR TIMING

Capacitors store charge and the basic formula is

$$V = \frac{Q}{C} \quad \text{Eq. 1}$$

where V is the voltage across a capacitor in Volts (abbreviated V), Q is the charge on the capacitor in Coulombs (abbreviated C), and C is the capacitance value in Farads (abbreviated F.) It turns out 1 F is a very large capacitor. The capacitors we will use are in the ranges of μF , nF , or pF . When a current runs into a capacitor, charge accumulates in it and the voltage across it increases. Consider the following circuit

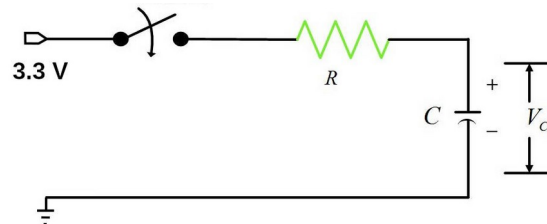


Figure 1: A charging RC circuit. If V_c starts at zero when the switch is closed, the capacitor will charge and V_c will increase. **Note** 3.3V is also called V_{cc} .

Challenge:

- If $R = 100 \text{ k}\Omega$ and $C = 100 \text{ }\mu\text{F}$, what will the initial current be?
- What do you think the maximum V_c will be when the capacitor is fully charged?

The Charge – Discharge Function

You should have seen the formula for a capacitor charging or discharging through a resistor

$$V(t) = V_0 \pm V_1 e^{-t/\tau} \quad \text{Eq. 2}$$

where $\tau = RC$.

Challenge:

- Find the value of τ in seconds for the Challenges above.
- Find the values for V_0 and V_1 for the circuit in Figure 1 when the switch is closed.

You are going to make an oscillator. Consider the circuit in Figure 2 (but don't build it yet.) You will drive the circuit with a digital output, and read V_C with an ADC input. You need to write a program that:

- Turns on the digital output to 1
- When $V_C = \frac{2}{3}V_{CC}$, set the digital output to 0
- When $V_C = \frac{1}{3}V_{CC}$, turn the digital output back 1.
- Repeat infinitely

Figure 3 shows what the waveform should look like, but t_{on} and t_{off} will be equal.

Super Challenge:

- How long will it take the RC circuit to charge from $\frac{1}{3}V_{CC}$ to $\frac{2}{3}V_{CC}$?
- What will T be in terms of R , C , and V_{CC} ?
- For $R = 100 \text{ k}\Omega$ and $C = 100 \text{ }\mu\text{F}$, what will T be?

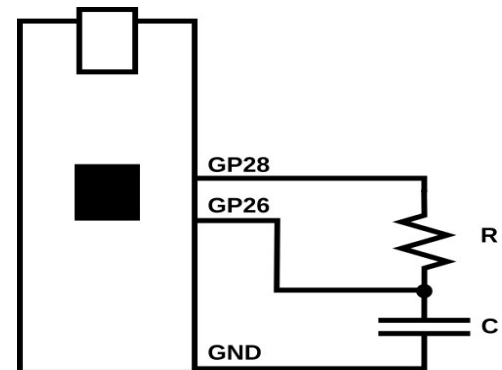


Figure 2: The oscillator circuit. GP28 is a digital output and GP26 is an ADC input.

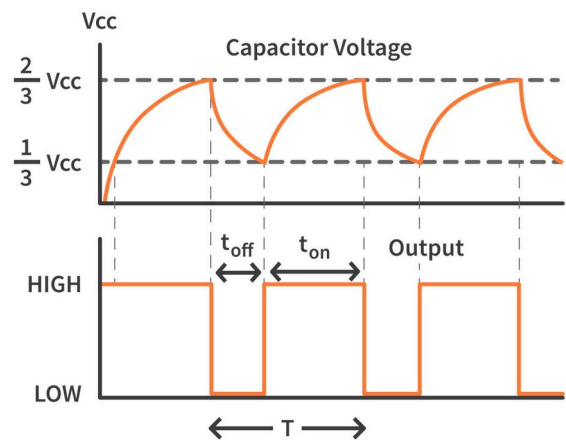


Figure 3: The charge-discharge curve for the oscillator. You must make t_{on} and t_{off} equal.

Building Your Oscillator

1) Build the oscillator circuit with the components above, program the PicoW, and measure its frequency using an oscilloscope. In the space below, analyze your data and compare it to your calculated T . What is the percentage difference?

2) Change the components to make a 1 kHz oscillator. Is the result within the tolerance of the components?
Show your work below.

To CONTINUE ...

The next lab is about using capacitors to filter signals in frequency. However, first you need to take a diversion to build a Function Generator. You will use it to make sine waves at different frequencies and measure how an RC filter affects that signal.

So now you will change gears to do Function Generator project.

MATERIALS

- Pico W on a breadboard.
- A 100 k Ω resistor
- A 100 μ F capacitor
- Variety of resistors and capacitor for students to try to make a 1 kHz oscillator.
- An oscilloscope.