

INTRODUCTION

A standard piece of equipment in an electronics lab is a *Function Generator*. A function generator creates variety waveforms (called functions) at variable frequencies.

In this lab you will build a function generator using a Pico W that you will use in future labs.

DESIGN OF FUNCTION GENERATOR

To make a function generator, first you need a way of creating continuous analog output. This is done using a DAC (Digital to Analog Converter). There are many DAC breakout boards you can use with microcontrollers. However, if you program in micropython, the microcontrollers are too slow to make waveforms faster than about 2 kHz.

Fortunately several people in the huge community of microcontroller/micropython users came up with a very clever solution for the PicoW: An R-2R DAC ladder coupled with two special features of the PicoW, **pio** and **dma**.

The R-2R Ladder

The R-2R ladder is a *parallel* device, which means that the data the microcontroller is sending has multiple, simultaneous data output lines. Figure 1 shows a 4-bit R-2R DAC. The simultaneous data input lines are **D0** – **D3**. Each of these can take on the values of either V_{cc} or 0.

You can analyze this circuit by setting all of the digital inputs to zero except one, and calculating **Vout**. Then you can use the principle of superposition to write the final **Vout** for any set of digital input values.

The easiest way to proceed is to use Thevenin's theorem, *Any network of voltage sources and resistors can be simplified to one voltage source in series with one resistor*.

You can also use Thevenin's theorem on a piece of a circuit, then successively on more and more of a circuit until you have the whole circuit analyzed.

Calculating The Thevenin Values

I will use the circuit in Figure 1 as an example.

First, we set D0 to V_{cc} , and the rest of the D's to ground.

Second, we highlight the bottom part of the circuit, inside the red line, and we will analyze this part first.

Voltage: Analyze the circuit using the normal rules for resistor circuits. This is just a 50% voltage divider, so $V_0 = \frac{1}{2} V_{cc}$.

Resistance: Set V_{cc} to ground and calculate the equivalent resistance between V_0 and ground. In this case two resistors of value $2R$ in parallel have an equivalent resistance of R .

Result: The circuit in red has a voltage source of $\frac{1}{2} V_{cc}$, and a series resistance of R .

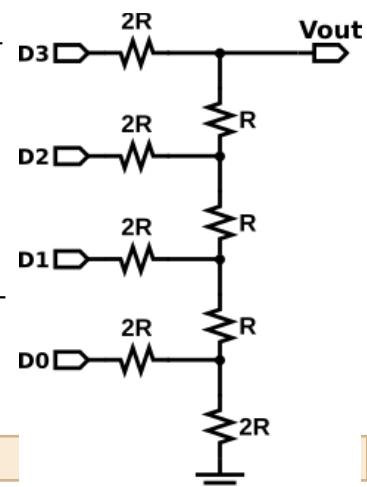


Figure 1: A four-bit R-2R DAC. Each of the digital outputs, D0 - D3 can take on the values of 3.3V or 0V.

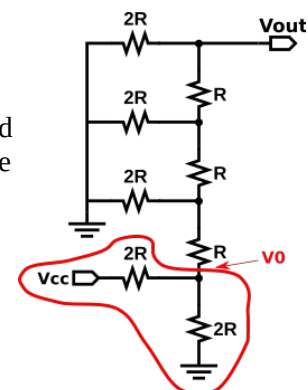


Figure 2: Start by setting D0 to V_{cc} , and the other digital inputs to ground. Next analyze the subcircuit in red.

With the red circuit replaced by its Thevenin equivalent, the circuit has reduced to the one in Figure 3.

Next analyze the circuit circled in green. Since the two resistors R are in series, they can be replaced by one resistor of value $2R$.

Now the green circuit is like the red circuit in Figure 2, so $V_1 = \frac{1}{4} V_{cc}$.

You can see this clever circuit is designed so you can keep working up the ladder, each time dividing the previous voltage by half.

Finally for this four-bit DAC, $V_{out} = \frac{1}{16} D_0$, where $D_0 = \text{either } 0 \text{ or } V_{cc}$.

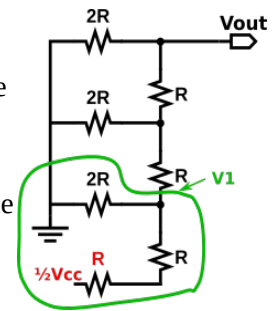


Figure 3: With the red circuit replaced by its Thevenin's equivalent, now analyze the green circuit.

Bit D1: Now we have to analyze what the effect of D_1 is on V_{out} . Like before, set $D_0 = V_{cc}$, and the other digital inputs to ground. This gives us the circuit in Figure 4. The two bottom resistors are two $2R$ resistors to ground, so they are equivalent to an R resistor to ground. That is then in series to an R resistor, so the three bottom resistors are equivalent to a $2R$ resistor to ground.

At this point the circuit, Figure 5, is similar to Figure 2 with one less “ladder rung”.

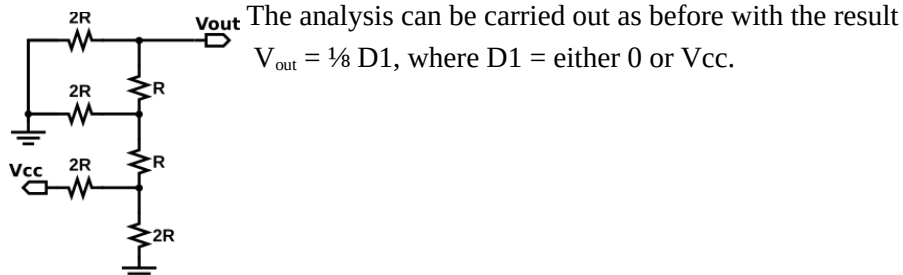


Figure 5: The D_1 circuit after replacing the bottom three resistors in Figure 4. This is similar to Figure 2, but with one less level.

The analysis can be carried out as before with the result $V_{out} = \frac{1}{8} D_1$, where $D_1 = \text{either } 0 \text{ or } V_{cc}$.

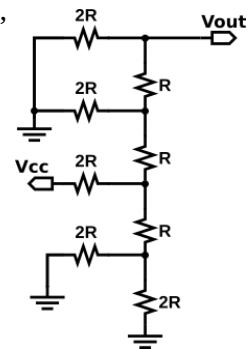


Figure 4: Analyzing D_1 . The bottom three resistors are equivalent to a $2R$ resistor to ground.

You can see the pattern develop and guess (correctly) $V_{out} = \frac{1}{4} D_2$, and $V_{out} = \frac{1}{2} D_3$.

The magic of superposition. Superposition states that the voltage across an element in a linear circuit is the algebraic sum of the voltage across that element due to *each* independent source acting alone. Since V_{out} is the voltage across the whole ladder, we can sum the contribution from each digital input. This gives

$$V_{out} = \frac{1}{2} D_3 + \frac{1}{4} D_2 + \frac{1}{8} D_1 + \frac{1}{16} D_0.$$

This is exactly what makes it a binary DAC. The output for $0xf$ is $\frac{15}{16} V_{cc}$. The output for $0x0$ is 0 V. There are 16 steps from 0 to $\frac{15}{16} V_{cc}$ in steps of $\frac{1}{16} V_{cc}$. The smallest step is called the LSD or *Least Significant Digit*.

Voltage & Time Digitization and DAC Resolution

This example is a 4-bit DAC. The voltage steps are $1/16$ th the total range of the DAC. You can easily see this by looking at the waveform with an oscilloscope. Instead of a nice smooth curve, you see a series of steps going up and down. Each step is one LSB (Least Significant Bit) in size. How can you do better? Add more inputs to the DAC.

The whole structure can be extended by adding four more R-2R sections and digital inputs to make an 8-bit DAC. This is what you are building in the DAC Project.

Why 8-bit? Because 8-bits gives you enough resolution to make a waveform that looks like a decent sine (or other type of) wave. I know sounds like a subjective judgment, but it comes from experience. You will see as you use the DAC that there are also “jumps” or “steps” in time called *time digitization*. The time digitization is set by how fast your microcontroller is, so a good engineering principle is to try to design your DAC so that the time and voltage digitization have about equal effects on the waveform generation.

BUILDING THE FUNCTION GENERATOR

The PCB (Printed Circuit Board) for the DAC is shown in Figure 6. All of the components will be mounted on this side, the front, of the PCB. The quick way to tell the front is that it has the board name, *FuncGen_24a* in the lower right corner. The Pico W and the op amp are not soldered to the board, but mounted in sockets. The finished board is in Figure 7. Figure 6 shows a finished PCB, except for the three connector sockets not yet done.

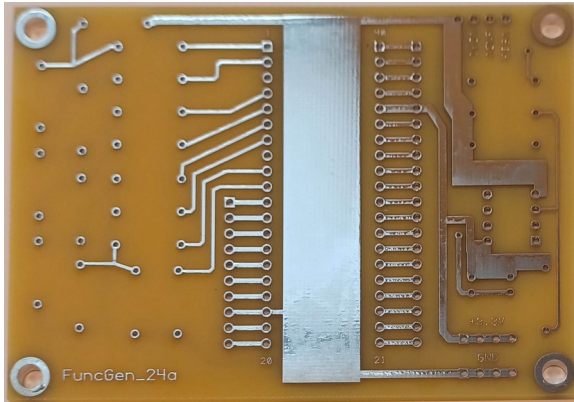


Figure 7: The DAC PCB.

It is hard to see the color codes on the resistors, so you can use Figure 8 to help place them.

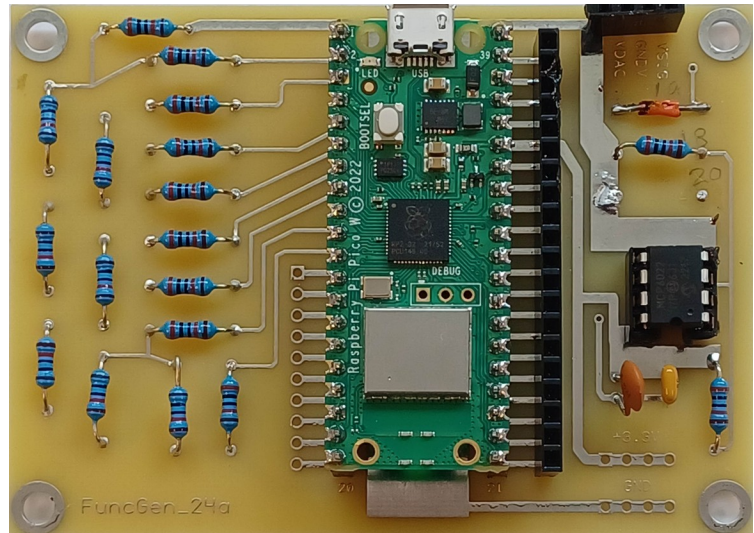


Figure 6: Finished PCB. The Pico W and the op amp are mounted in their sockets.

Note that R19 is missing. It is replaced by a wire just above R18. Below R18 are two pads that are not used.

Assembly.

- Start by mounting the resistors. *Pay close attention to the values!!!*
- Bend the leads so the wires can fit through the mounting holes.
- Put the wires through the holes and pull the wires from the opposite side until the resistor is close to the PCB.
- Flip the board over and solder the wires to the pad.
- Clip off the extra wire.
- I usually do two to four resistors at a time.
- For the Pico W sockets, plug the Pico W into the sockets then place the sockets in the PCB. Then solder them in place.

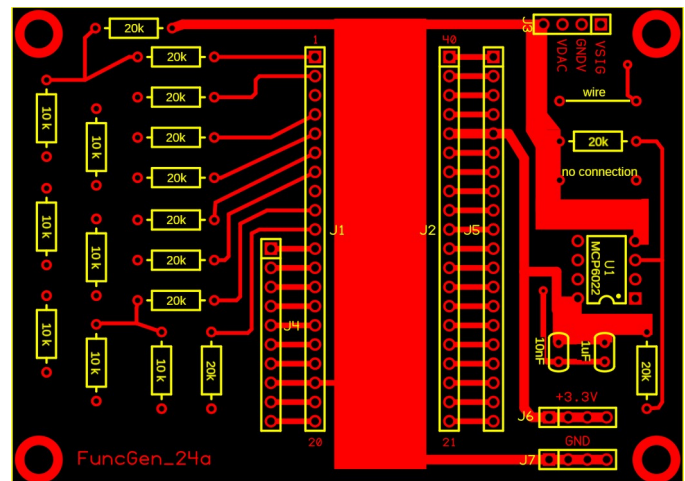


Figure 8: A key to placing components on the PCB.

USING THE WAVEFORM GENERATOR

Plug the waveform generator into you laptop and use Thonny to connect to it. Note you can make sine waves with a starting frequency, ending frequency, number of frequencies. There are three outputs from the function generator, Signal (SIG), Signal Ground (GND_S), and Ground (GND.) Since the Pico W runs on positive 3.3 V, the function generator makes a signal ground half way between the maximum SIG and GND. Relative to GND_S, the sine waves are an AC (Alternating Current) signal. If you measure using ADC *both* SIG and GND_S and subtract them, you can measure the signal as an AC signal. The Figure

APPENDIX – EXPLANATION OF R-2R LADDER USING THÉVENIN'S THEOREM

Thévenin's Theorem states, "Any linear electrical network containing only voltage sources, and resistances can be replaced at terminals A–B by an equivalent combination of a voltage source V_{th} in a series connection with a resistance R_{th} ." Figure 2 shows an example.

The Thévenin equivalent resistance is calculated by replacing any voltage sources in the system with a short circuit, then calculating the resistance using the formulas for series and parallel circuits.

The Thévenin equivalent voltage is calculated by calculating the voltage at the output, often using the principle of a voltage divider.

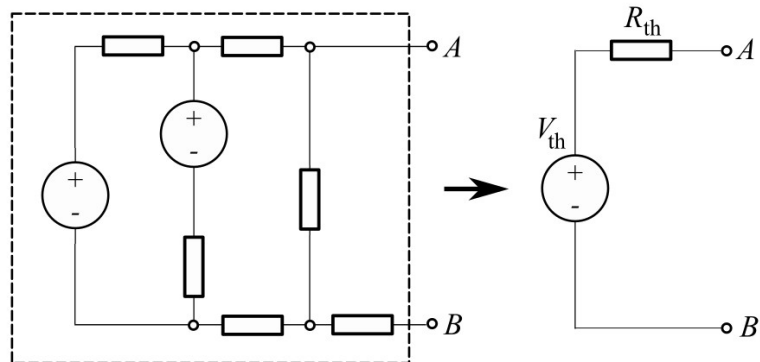


Figure 9: Illustration of Thévenin's Theorem. The two voltage sources and six resistors can be replaced by one voltage in series with a resistor.

Another great help for analyzing the R-2R circuit is the theorem of superposition. *The electrical voltage at every point in the system through which the current flows is equal to the algebraic sum of those voltages which each of the voltage sources would produce independently of the others.* This means we can analyze V_{out} for each digital input independently, then add them together for the final answer.

Start by setting **D3** to $V_{pwr} = 3.3V$ and the other digital inputs to zero (ground.) Then the bottom two $2R$ resistors are parallel to ground, red in Figure 3, so you can replace them with one resistor of value R . That gives us the equivalent circuit in Figure 4.

This circuit is just like the original circuit but one digital input less. (Remember **D0** to **D2** = 0 for this.) This can be repeated two more times giving the circuit in Figure 5.

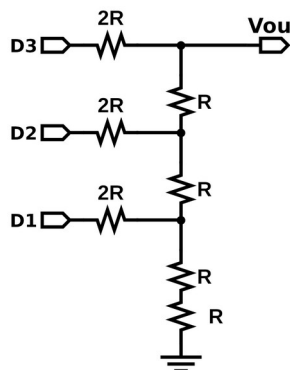


Figure 11: The equivalent circuit. Note this is similar to the starting circuit with one less digital input.

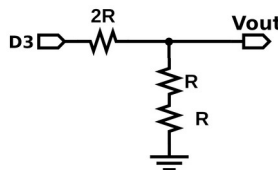


Figure 12: The final equivalent circuit. This is now a voltage divider with ratio $\frac{1}{2}$ between V_{pwr} and V_{out} .

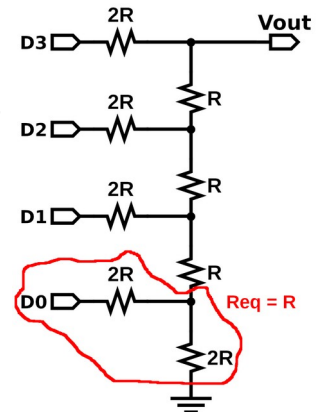


Figure 10: The two resistors in the red circle are two resistors of value $2R$ in parallel. The equivalent resistance is R .

This final equivalent circuit is a voltage divider with equal legs of $2R$, so

$$V_{out} = \frac{1}{2} V_{pwr} \quad . \quad \text{Since } \mathbf{D3} \text{ can only be } 0 \text{ or } V_{pwr}, \text{ the formula can be written}$$

$$V_{out} = V_{pwr} \frac{1}{2} D3$$

Next consider the case where $D_2 = V_{pwr}$, and the rest of the digital inputs are zero. The circuit can be redrawn as in Figure 6. The five resistors on the right can be replaced by a resistor of value $2R$ to ground, Figure 7. Then the network inside the red line can be reduced to a voltage of $\frac{1}{2} D_2$ in series with a resistor of value R .

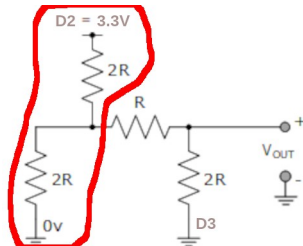


Figure 14: The previous figure is equivalent with this circuit. The network inside the red line is equivalent to $\frac{1}{2} D_2$ in series with R .

Finally the circuit is equivalent to Figure 8 which is a voltage divider from $\frac{1}{2} D_2$ to ground with a ratio of 0.5, so

$$V_{out} = V_{pwr} \frac{1}{4} D_2$$

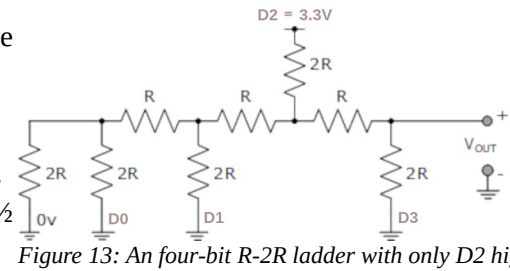


Figure 13: An four-bit R-2R ladder with only D_2 high.

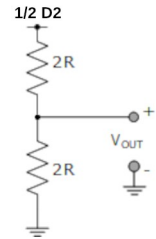


Figure 15: The final equivalent circuit. $V_{out} = \frac{1}{4} D_2$.

Repeating this process for the last two digital outputs gives

$$V_{out} = V_{pwr} \frac{1}{8} D_1 \quad \text{and} \quad V_{out} = V_{pwr} \frac{1}{16} D_0$$

Now the superposition theorem allows us to simply add these results together giving

$$V_{out} = V_{pwr} \left(\frac{1}{2} D_3 + \frac{1}{4} D_2 + \frac{1}{8} D_1 + \frac{1}{16} D_0 \right)$$

This gives 16 values ranging from 0 to $\frac{15}{16} V_{pwr}$ in steps of $\frac{1}{16} V_{pwr}$.